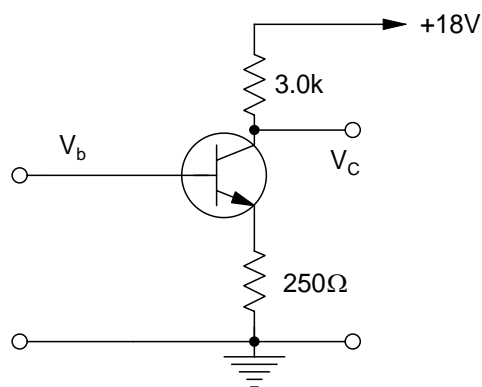



Sketched below is a circuit including a typical NPN silicon transistor.

- a. For the case $V_b = 1.7 \text{ volts}$, calculate the **voltages** at the **emitter** and **collector** of the transistor, and calculate the (estimated) **base current**.
- b. Calculate the **base voltage** and (estimated) **base current** necessary to make the **collector voltage** = 12 V .




Sketched below is a circuit including a typical NPN silicon transistor.

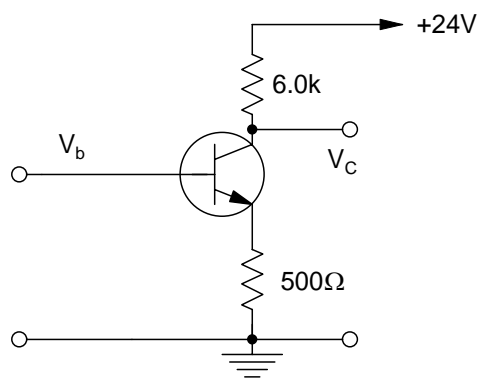- a. For the case $V_b = 1.4 \text{ volts}$, calculate the **voltages** at the **emitter** and **collector** of the transistor, and calculate the (estimated) **base current**.
- b. Calculate the **base voltage** and (estimated) **base current** necessary to make the **collector voltage** = 15 V .



Sketched below is a circuit including a typical NPN silicon transistor.

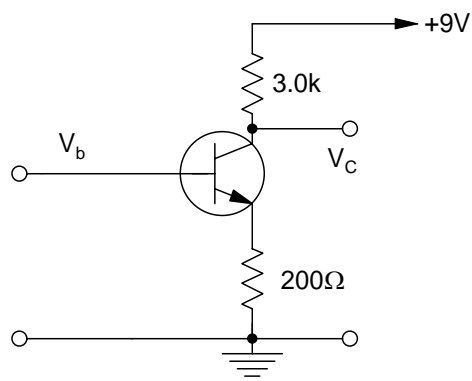- a. For the case $V_b = 1.1 \text{ volts}$, calculate the **voltages** at the **emitter** and **collector** of the transistor, and calculate the (estimated) **base current**.
- b. Calculate the **base voltage** and (estimated) **base current** necessary to make the **collector voltage** = 6 V .







Design a “standard” transistor amplifier circuit using an 18 V power supply to meet the specifications: $R_{out} \leq 3.0k$, $A \geq 12$, and $R_{in} \geq 12k$. (You should *sketch the circuit* and your answers should consist of values for the following: R_C , R_E , R_{B1} , R_{B2} , V_C , V_E , V_B , I_C , and I_B . Also, your values for R_{B1} and R_{B2} should be calculated with the estimated I_B taken into account.)





Design a “standard” transistor amplifier circuit using a 24 V power supply to meet the specifications: $R_{out} \leq 2.5k$, $A \geq 10$, and $R_{in} \geq 15k$. (You should *sketch the circuit* and your answers should consist of values for the following: R_C , R_E , R_{B1} , R_{B2} , V_C , V_E , V_B , I_C , and I_B . Also, your values for R_{B1} and R_{B2} should be calculated with the estimated I_B taken into account.)

Design a “standard” transistor amplifier circuit using a 9 V power supply to meet the specifications: $R_{out} \leq 2.7k$, $A \geq 15$, and $R_{in} \geq 10k$. (You should *sketch the circuit* and your answers should consist of values for the following: R_C , R_E , R_{B1} , R_{B2} , V_C , V_E , V_B , I_C , and I_B . Also, your values for R_{B1} and R_{B2} should be calculated with the estimated I_B taken into account.)





For the circuits sketched below, the output voltage of the “typical” operational amplifier is restricted to the range $-V_{Lim} \leq V_{out} \leq +V_{Lim}$. For both cases, sketch the output waveform on the graphs labeled “**Output Volts**” (below the sketch of the sine wave input voltage). (The horizontal dashed lines on the output graphs indicate the output voltage limits, $\pm V_{Lim} = \pm 12V$.) The output waveform must include labels indicating voltage values and vertical lines between the input and output graphs should “key” the output waveform to the input. (*Examine the circuits carefully!!!*)

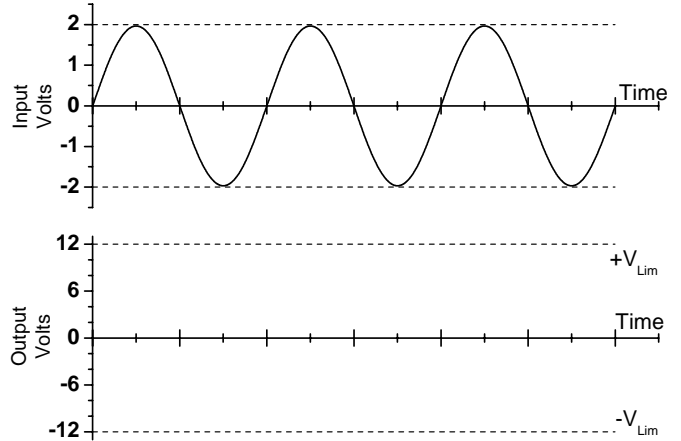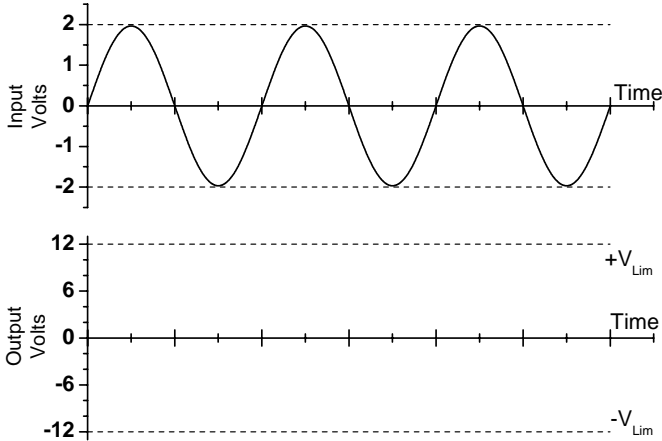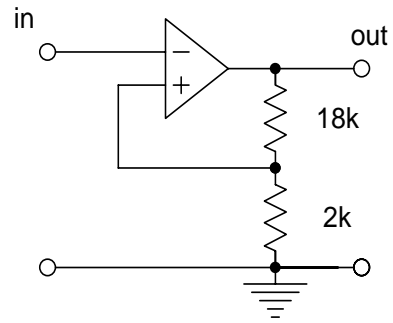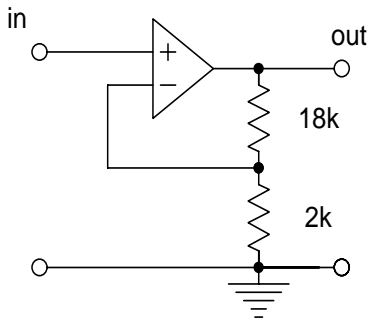





For the circuits sketched below, the output voltage of the “typical” operational amplifier is restricted to the range $-V_{Lim} \leq V_{out} \leq +V_{Lim}$. For both cases, sketch the output waveform on the graphs labeled “**Output Volts**” (below the sketch of the sine wave input voltage). (The horizontal dashed lines on the output graphs indicate the output voltage limits, $\pm V_{Lim} = \pm 18V$.) The output waveform must include labels indicating voltage values and vertical lines between the input and output graphs should “key” the output waveform to the input. (*Examine the circuits carefully!!!*)

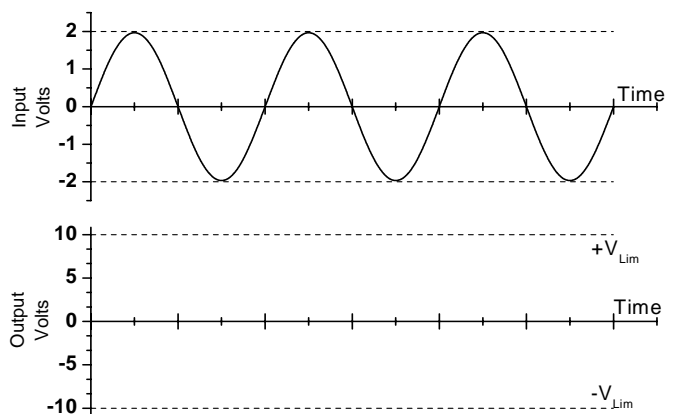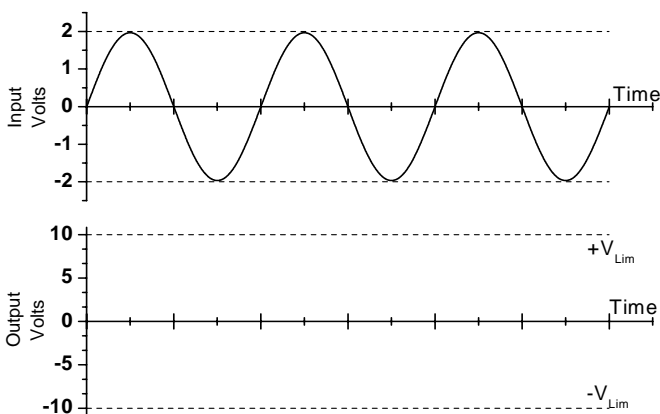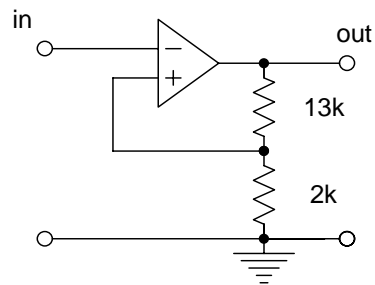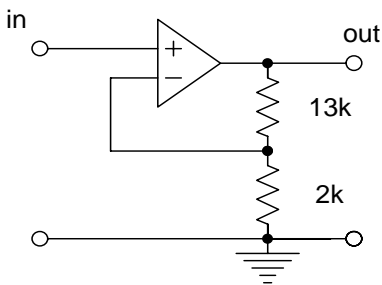


For the circuits sketched below, the output voltage of the “typical” operational amplifier is restricted to the range $-V_{Lim} \leq V_{out} \leq +V_{Lim}$. For both cases, sketch the output waveform on the graphs labeled “**Output Volts**” (below the sketch of the sine wave input voltage). (The horizontal dashed lines on the output graphs indicate the output voltage limits, $\pm V_{Lim} = \pm 10V$.) The output waveform must include labels indicating voltage values and vertical lines between the input and output graphs should “key” the output waveform to the input. (*Examine the circuits carefully!!!*)

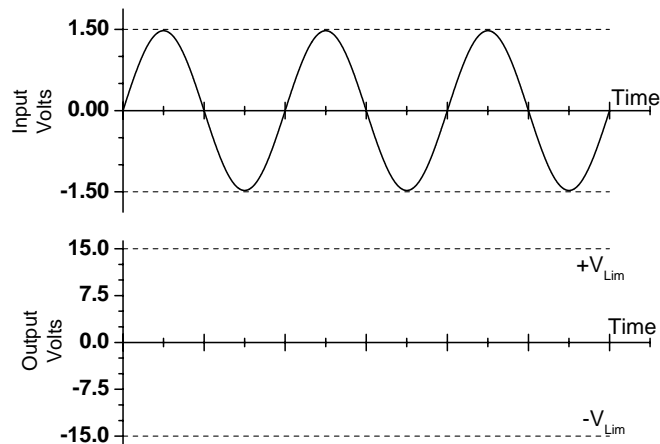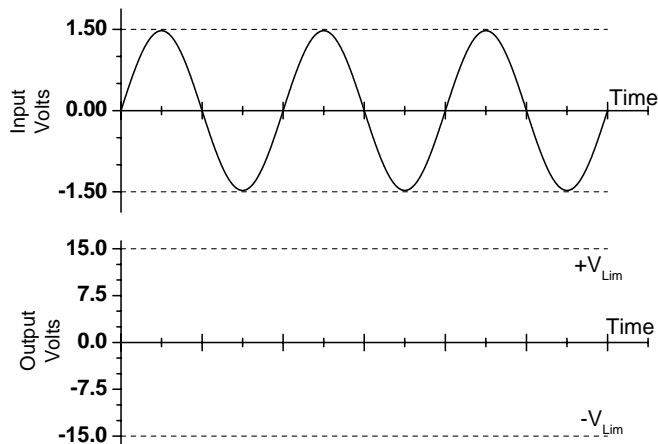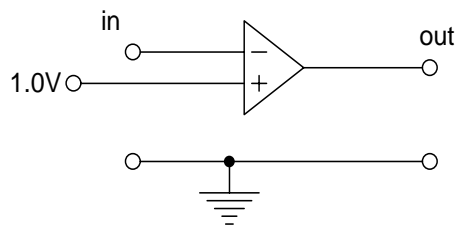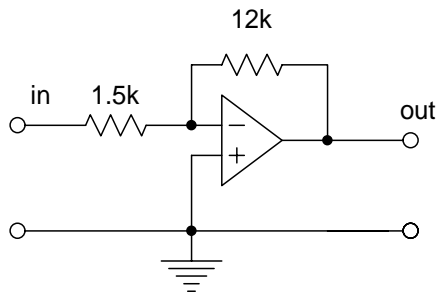


For the circuits sketched below, the output voltage of the ideal operational amplifier is restricted to the range $-V_{Lim} \leq V_{out} \leq +V_{Lim}$. For both cases, sketch the output waveform on the graphs labeled “**Output Volts**” (below the sketch of the sine wave input voltage). (The horizontal dashed lines on the output graphs indicate the output voltage limits, $\pm V_{Lim} = \pm 15V$.) The output waveform must include labels indicating voltage values and must include vertical lines to clearly show the time relationship between the input and output graphs. (*Examine the circuits carefully!!!*)

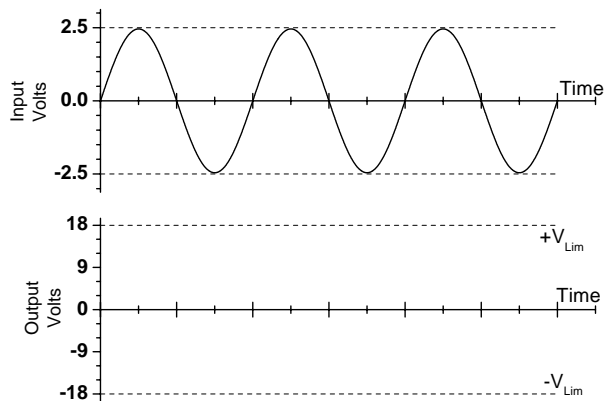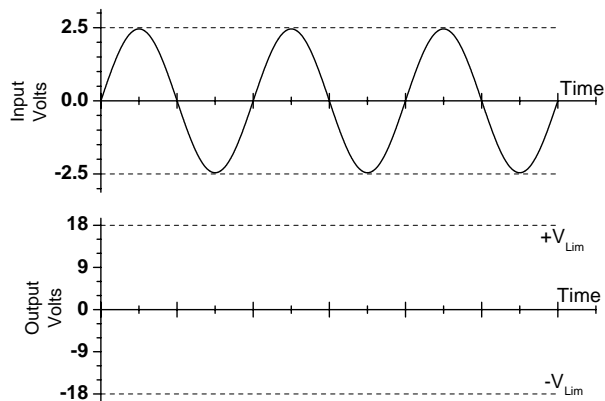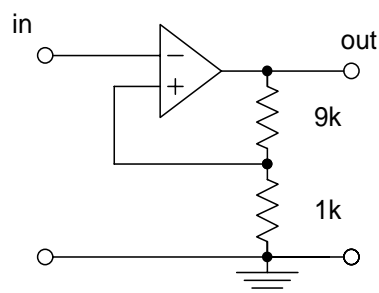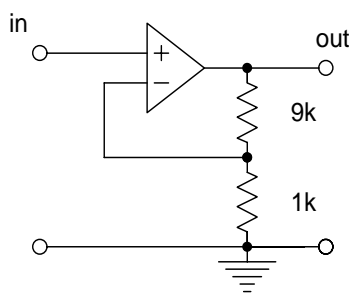

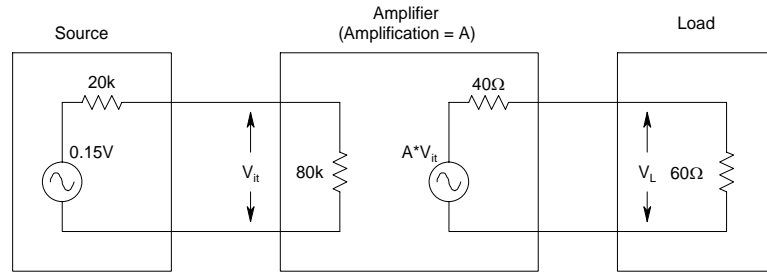
For the amplifier system sketched below, calculate the minimum value of the amplification (A) needed to obtain voltage across the load (V_L) of **12 Volts**.



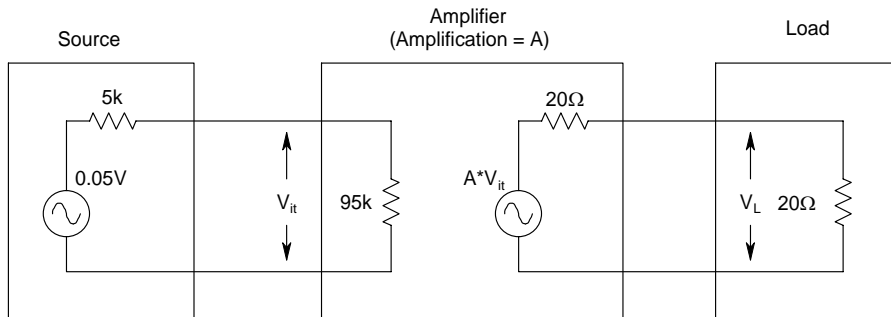For the amplifier system sketched below, calculate the minimum value of the amplification (A) needed to obtain voltage across the load (V_L) of **6 Volts**.



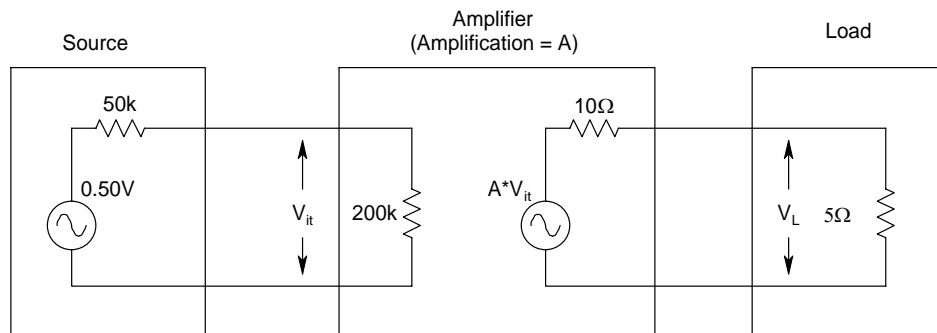For the amplifier system sketched below, calculate the minimum value of the amplification (A) needed to obtain voltage across the load (V_L) of **10 Volts**.



Design and sketch a circuit *using no more than 2 operational amplifiers* to combine the *variable* input voltages (V_1 , V_2 , and V_3) and the *constant* input $-15V$ to give the output:

$$V_{out} = 3V_1 + 4V_2 - 2V_3 + 5\text{volts}$$





Design and sketch a circuit *using no more than 2 operational amplifiers* to combine the *variable* input voltages (V_1 , V_2 , and V_3) and the *constant* input $+5V$ to give the output:

$$V_{out} = 4V_1 - V_2 + 5V_3 - 7\text{volts}$$

Design and sketch a circuit *using no more than 2 operational amplifiers* to combine the *variable* input voltages (V_1 , V_2 , and V_3) and the *constant* input $-12V$ to give the output:


$$V_{out} = 5V_1 - 3V_2 + 2V_3 - 3\text{volts}$$

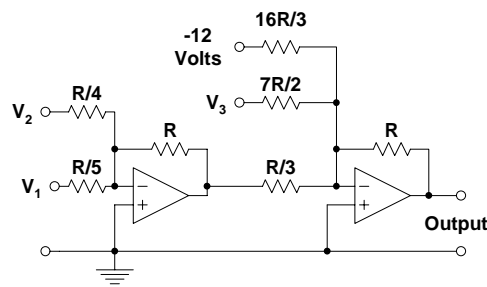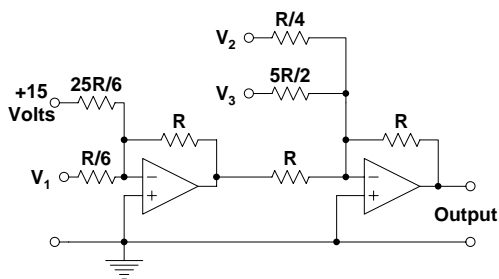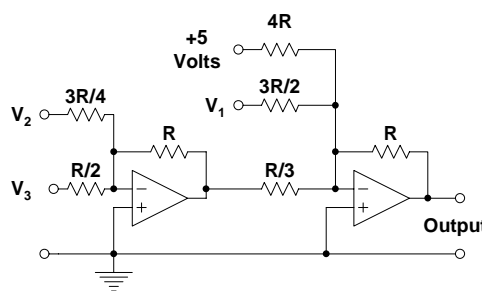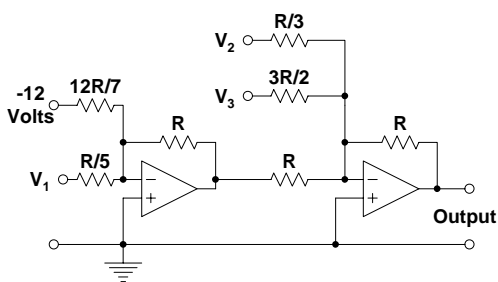Write the relationship between output and the *variable* and constant input voltages (V_1 , V_2 , and V_3) for the circuits sketched below. (*Pay careful attention to the components.*)




Sketched below is a circuit incorporating an amplifier in the “non-inverting” configuration used for operational amplifiers. The “**basic amplifier relation,**” is $V_{out} = A(V_+ - V_-)$. Use this relation to calculate the following: (You may assume the input resistance of the amplifier to be sufficiently high that negligible current enters it.)

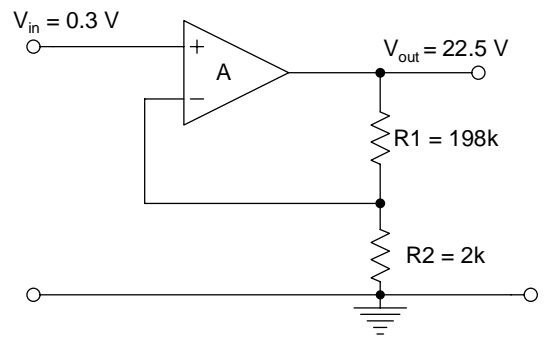- The **minimum** value of A necessary for the input shown to generate the output shown.
- The **output voltage** for very large values of A (approaching ∞).




Sketched below is a circuit incorporating an amplifier in the “non-inverting” configuration used for operational amplifiers. The “**basic amplifier relation,**” is $V_{out} = A(V_+ - V_-)$. Use this relation to calculate the following: (You may assume the input resistance of the amplifier to be sufficiently high that negligible current enters it.)

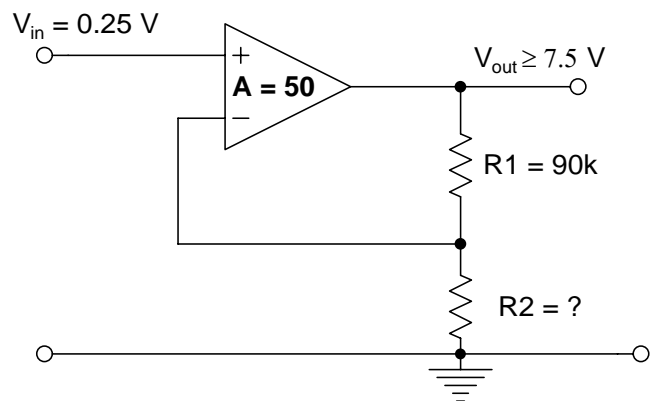- The **minimum** value of R_1 necessary for the input shown to generate the output shown.
- The **output voltage** (using the R_2 value shown and the value of R_1 calculated above) for very large values of A (approaching ∞).



Sketched below is a circuit incorporating an amplifier in the “non-inverting” configuration used for operational amplifiers. The “**basic amplifier relation,**” is $V_{out} = A(V_+ - V_-)$. Use this relation to calculate the following: (You may assume the input resistance of the amplifier to be sufficiently high that negligible current enters it.)

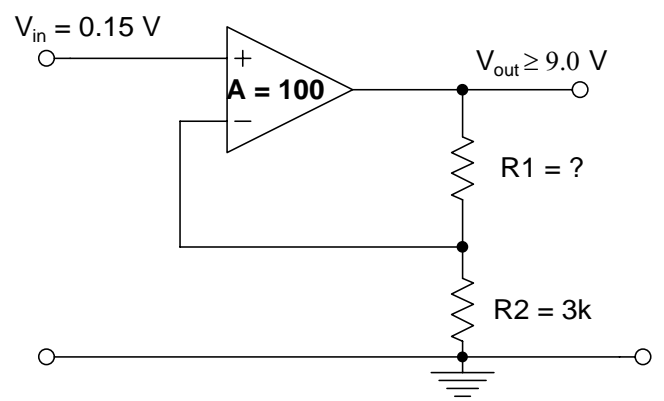- The **minimum** value of R_1 necessary for the input shown to generate the output shown.
- The **output voltage** (using the R_2 value shown and the value of R_1 calculated above) for very large values of A (approaching ∞).



Sketched below is a circuit incorporating an amplifier and a transistor in the configuration used for voltage regulators.

- The “**basic amplifier relation,**” is $V_{OA} = A(V_+ - V_-)$. Use this relation to calculate V_{out} for the case $V_{in} = 0.25 V$, $R_1 = 95k$, $R_2 = 5k$, and $A = 15$. In this calculation, you **MUST** include the transistor’s base-emitter voltage, V_{BE} . (You may assume the input resistance of the amplifier to be sufficiently high that negligible current enters it.)
- Calculate the output for the input voltage and resistors in (a) when $A \rightarrow \infty$.
- Calculate the value of A needed to make the result in (a) 90% of the value in (b).

