
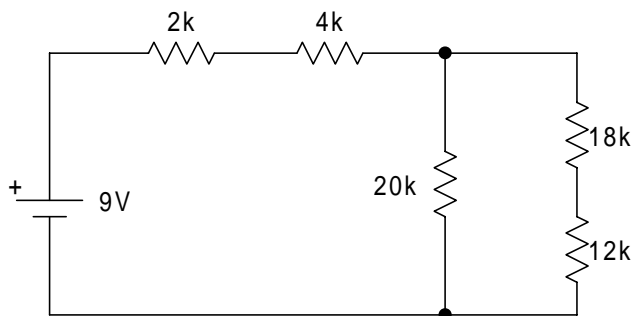


ELECTRONICS HOMEWORK SET #1

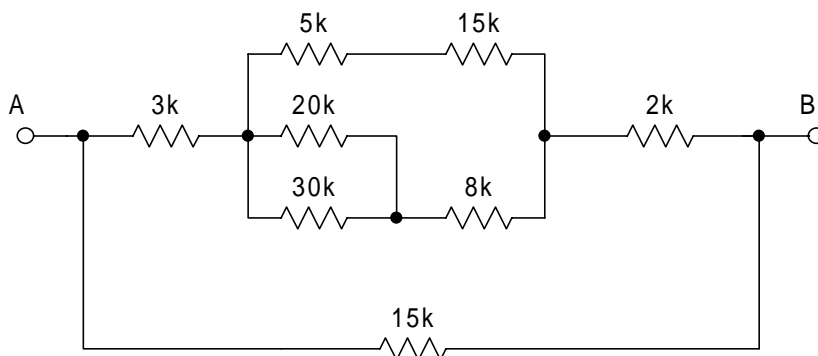
- 1) For the circuit shown, calculate the current in each resistor, and calculate the voltage across each resistor:




- 2) Calculate the equivalent resistance between points A and B for the circuit shown below:



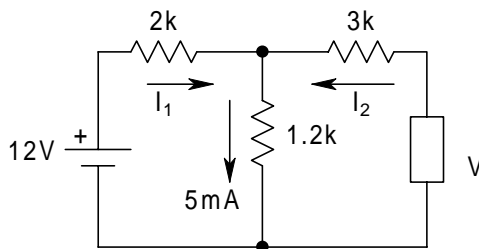- 3) Use Kirchoff's rules to evaluate the currents I_1 , I_2 , and the voltage V in the circuit below:



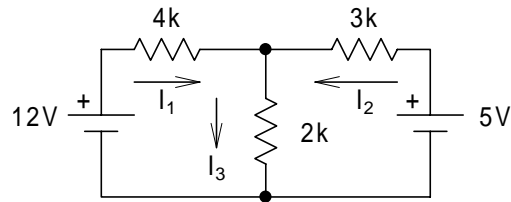- 4) Use the principle of superposition to evaluate the currents in the circuit shown below:



- 5) Evaluate the voltage indicated by V_x on the diagram below for the following values of R_x :

a) $R_x \rightarrow \infty$ (open circuit)

b) $1\text{M}\Omega$


c) $10\text{K}\Omega$

d) $1\text{K}\Omega$

e) 100Ω

f) 1Ω

g) 0Ω (short circuit)

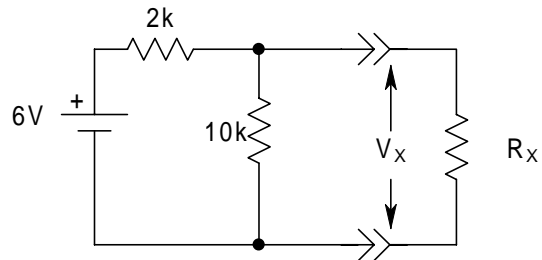

- 6) In the previous problem, the symbol "———>>———" represents terminals (with removable connections, such as banana plugs and jacks). Calculate the Thevenin voltage and resistance for the terminals indicated (excluding R_x).

- 7) Use Kirchoff's Laws to evaluate the currents in the circuit of problem 4.

- 8) Use Thevenin's theorem to evaluate the current I_3 in the circuit of problem 4.