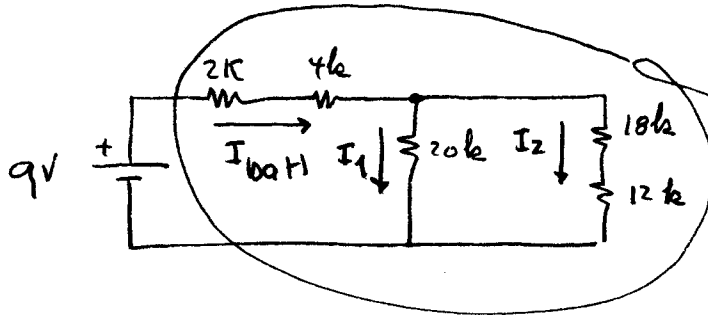


Electronics, H.W. Set 1

1.)



$$R_{eq} = [2k \text{ series } 4k] \text{ series } [20k // (18k \text{ series } 12k)]$$

$$I_{batt} = \frac{9V}{18k} = \frac{1}{2} \text{ mA} = I_{2k} = I_{4k}$$

$$V_{2k} = \left(\frac{1}{2} \text{ mA}\right) (2k) = 1V$$

$$V_{4k} = \left(\frac{1}{2} \text{ mA}\right) (4k) = 2V$$


$$I_2 = \frac{V_{20k}}{30k} = \frac{6V}{30k} = \frac{1}{5} \text{ mA}$$

$$V_{20k} = 9V - (V_{2k} + V_{4k}) = 6V \quad ; \quad I_{20k} = \frac{V_{20k}}{20k} = \frac{6}{20} \text{ mA} = .3 \text{ mA} = I_1$$

$$V_{18k} = 18k (I_2) = 18k \left(\frac{1}{5} \text{ mA}\right) = 3.6V$$


$$V_{12k} = 12k (I_2) = 12k \left(\frac{1}{5} \text{ mA}\right) = 2.4V$$

2.)

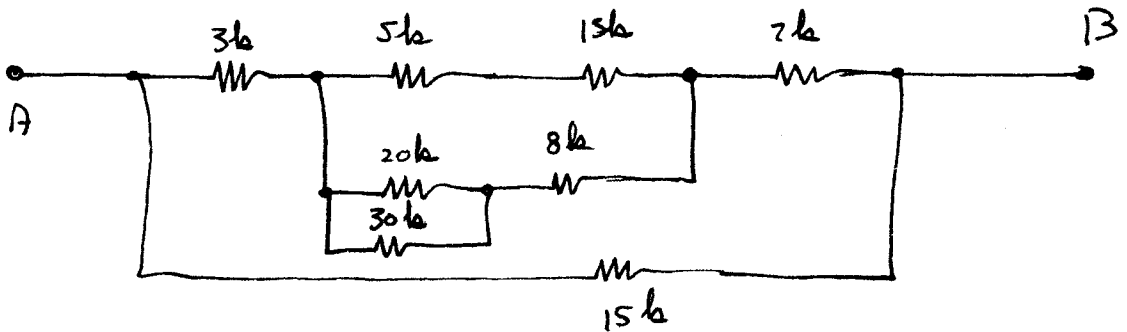

$$\left. \begin{array}{l} (20k // 30k) \text{ series } 8k = R_1 = 20k \\ 5k \text{ series } 15k = R_2 = 20k \end{array} \right\} R_1 // R_2 = 20k // 20k = 10k$$

$$R_{AB} = [3k \text{ series } (R_1 // R_2) \text{ series } 7k] // 15k = 15k // 15k = 7.5k$$

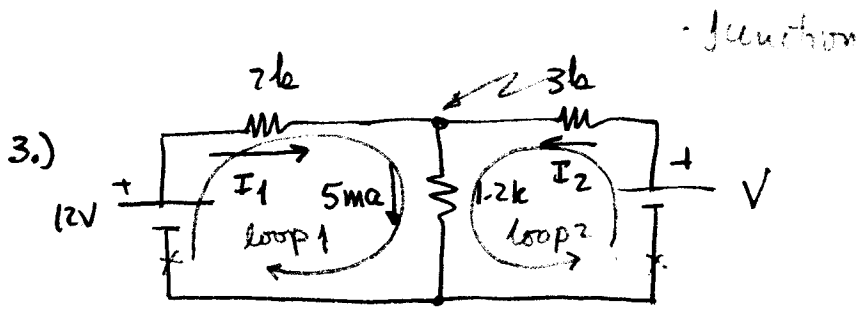


loop 1:  $0 = 12V - 2kI_1 - (5ma)(1.2k) \rightarrow 6V = 2kI_1 \rightarrow I_1 = +3ma$

loop 2:  $0 = V - 3kI_2 - (5ma)(1.2k)$


Junction:  $I_1 + I_2 = 5ma \rightarrow I_2 = 5ma - 3ma = +2ma$

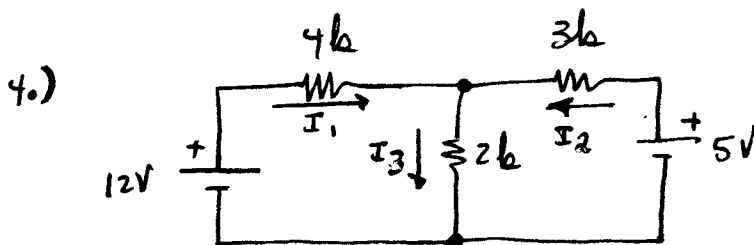$V = 3kI_2 + 6V = (3k)(2ma) + 6V = 6V + 6V = +12V$




superposition

Partial Circuit  
"A"

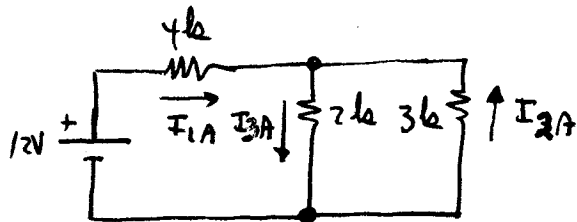

$I_{1A} = \frac{12V}{5.2k} = 2.31 ma$   
 $I_{3A} = 1.38 ma$   
 $I_{2A} = -0.92 ma$   
*note arrow!*

Partial Circuit  
"B"

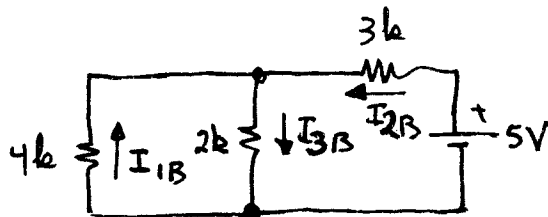


$I_{2B} = \frac{5V}{4\frac{1}{3}k} = 1.15 ma$   
 $I_{3B} = 0.77 ma$   
 $I_{1B} = -0.38 ma$   
*note the arrow!*

$I_3 = I_{3A} + I_{3B} = (0.77 + 1.38) ma = 2.15 ma$

$I_2 = I_{2A} + I_{2B} = (-0.92 + 1.15) ma = 0.23 ma$

$I_1 = I_{1A} + I_{1B} = (2.31 - 0.38) ma = 1.93 ma$

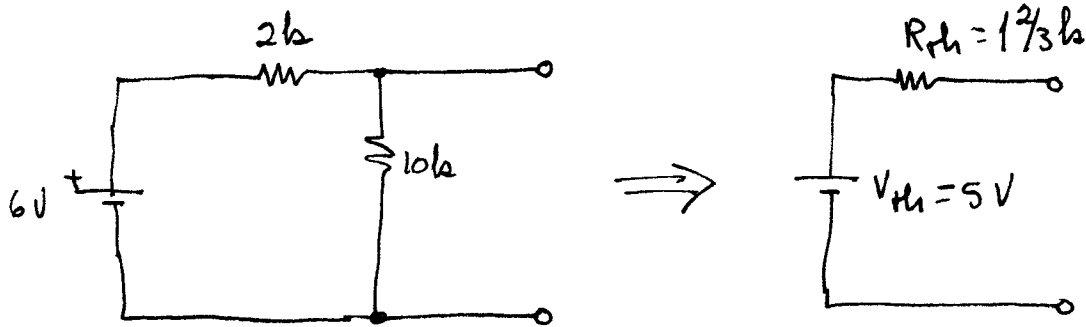
5. + 5.) the easiest method is to work #6 first:



$$V_{th} = \frac{6V}{12k} \cdot 10k = \underline{5V}$$

$$R_{th} = 2k // 10k = \frac{10k}{6} = \underline{1\frac{2}{3}k}$$

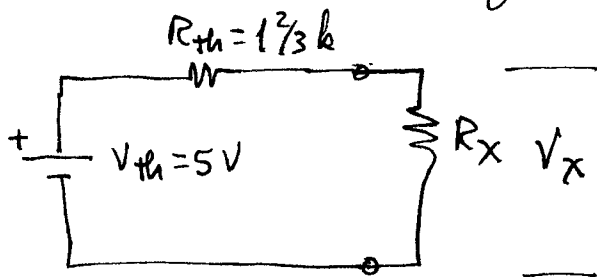to find  $V_x$ , the equivalent circuit is



$$V_x = \left( \frac{V_{th}}{R_{th} + R_x} \right) R_x$$

a.)  $V_x = V_{th} = \underline{5V}$  ( $R_x = \infty$ )

f.)  $V_x = \left( \frac{5V}{1\frac{2}{3}k + 1\Omega} \right) 1\Omega = \underline{0.003V}$

b.)  $V_x = \left( \frac{5V}{1\frac{2}{3}k + 1M} \right) 1M \approx \underline{5V}$


c.)  $V_x = \left( \frac{5V}{1\frac{2}{3}k + 10k} \right) 10k = \underline{4.29V}$

g.)  $V_x = \left( \frac{5V}{1\frac{2}{3}k} \right) 0 = \underline{0}$

d.)  $V_x = \left( \frac{5V}{1\frac{2}{3}k + 1k} \right) 1k = \underline{1.87V}$

e.)  $V_x = \left( \frac{5V}{1\frac{2}{3}k + 0.1k} \right) 0.1k = \underline{0.28V}$

Set 1, P. 4

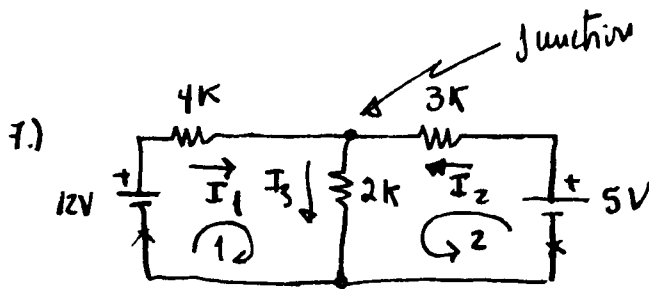

KVL

① loop 1:  $0 = 12V - I_1 \cdot 4k - I_3 \cdot 2k$

② loop 2:  $0 = 5V - 3kI_2 - 2kI_3$

KCL

③ junction:  $I_1 + I_2 = I_3$

①+③

$0 = 12V - I_1 \cdot 4k - (I_1 + I_2) \cdot 2k$  ④

②+③  $0 = 5V - 3kI_2 - 2k(I_1 + I_2)$  ⑤

④:  $0 = 12 - 6kI_1 - 2kI_2 \rightarrow I_1 = \frac{12 - 2kI_2}{6k} = \frac{6 - kI_2}{3k}$


④+⑤  $0 = 5V - 5kI_2 - 2kI_1 = 5V - 5kI_2 - 2k \left[ \frac{(12 - 2kI_2)}{6k} \right]$

$0 = 5V - 4V - I_2 \left( 5k - \frac{4}{6}k \right)$


$\therefore I_2 = \frac{1V}{4\frac{1}{3}k} = 0.23 \text{ ma}$

$I_1 = 1.92 \text{ ma}$

$I_3 = 2.15 \text{ ma}$

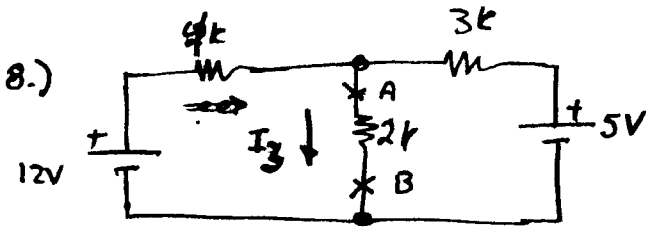

$2k$   
removed  
 $\Rightarrow$

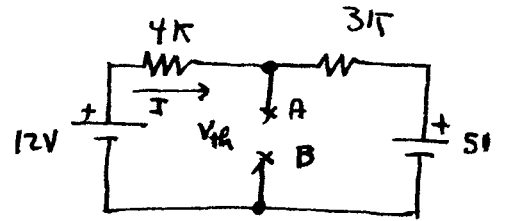

$$V_{th} = 12V - I(4k)$$


$$= 12V - 4V = 8V$$

$$; \quad \text{I: } 0 = 12V - I4k - I3k - 5$$

$$I = \frac{7V}{7k} = 1mA$$

$$R_{th} = 4k // 3k = 12k/7$$

net result

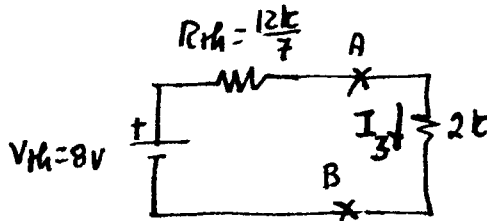

$$I_3 = \frac{8V}{2k + \frac{12k}{7}} = \frac{56}{26} = 2.15 mA$$