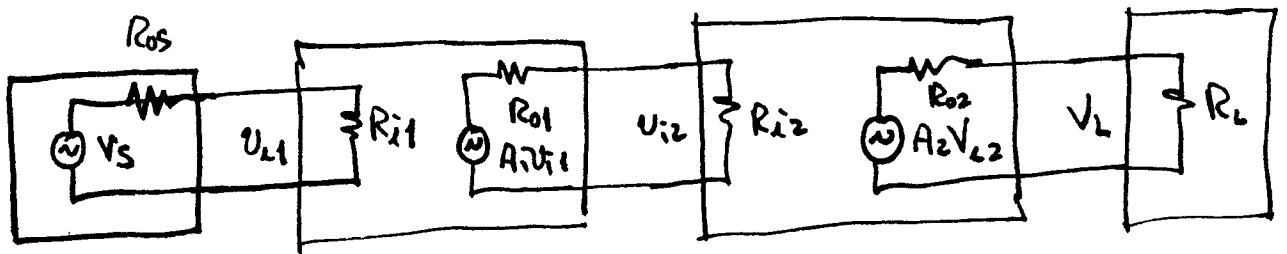


Phys 350/890
Homework Set #4

1.)



$\epsilon_A = \frac{V_L}{V_s}$. From analysis of each loop:

$$V_{i1} = \left(\frac{V_s}{R_{os} + R_{i1}} \right) R_{i1} = V_s \left(\frac{R_{i1}}{R_{os} + R_{i1}} \right)$$

$$V_{i2} = \left(\frac{A_1 V_{i1}}{R_{o1} + R_{i2}} \right) R_{i2} = A_1 V_{i1} \left(\frac{R_{i2}}{R_{o1} + R_{i2}} \right) = A_1 V_s \left(\frac{R_{i1}}{R_{os} + R_{i1}} \right) \left(\frac{R_{i2}}{R_{o1} + R_{i2}} \right)$$

$$V_L = \left(\frac{A_2 V_{i2}}{R_{o2} + R_L} \right) R_L = A_2 V_{i2} \left(\frac{R_L}{R_{o2} + R_L} \right) = A_2 A_1 V_s \left(\frac{R_{i1}}{R_{os} + R_{i1}} \right) \left(\frac{R_{i2}}{R_{o1} + R_{i2}} \right) \left(\frac{R_L}{R_{o2} + R_L} \right)$$

thus,

$$\epsilon_A = \frac{V_L}{V_s} = A_1 A_2 \left(\frac{R_{i1}}{R_{os} + R_{i1}} \right) \left(\frac{R_{i2}}{R_{o1} + R_{i2}} \right) \left(\frac{R_L}{R_{o2} + R_L} \right)$$

set #4, P.2 cont

applying the result to the cases given :

$$A_{\text{effective}} = \frac{V_L}{V_S} = A_1 A_2 \left(\frac{R_{in1}}{R_{os} + R_{in1}} \right) \left(\frac{R_{o2}}{R_{e2} + R_{in2}} \right) \left(\frac{R_L}{R_{o2} + R_L} \right)$$

a.) $A_{\text{effective}} = 200 \left(\frac{10k}{10k + 1k} \right) \left(\frac{50k}{50k + 1k} \right) \left(\frac{100}{100 + 10} \right) =$


$$\boxed{E.A. = 181}$$

b.) $E.A. = 200 \left(\frac{1k}{1k + 10k} \right) \left(\frac{100}{100 + 100} \right) \left(\frac{10}{10 + 10} \right)$

$$\boxed{E.A. = 4.55}$$

Homework Set #4

2.)

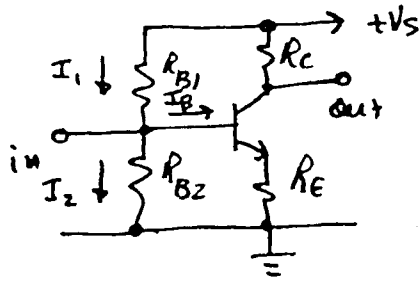

• $A \geq 15$: CHOOSE $A = 15$

$$A = \frac{R_c}{R_e} \Rightarrow \frac{R_c}{R_e} = 15$$

• $R_{out} \leq 3k$: CHOOSE $R_{out} = 3k$

$$R_{out} = R_c = 3k$$

$$R_e = \frac{R_c}{A} = \frac{3k}{15} = 200\Omega$$

• Aim for $V_c = \frac{V_s}{2} = \frac{15V}{2} = 7.5V$ at No-Signal:

need $I_c = \frac{V_{RC}}{R_c} = \frac{V_s - V_c}{R_c} = \frac{7.5V}{3k} = 2.5mA$

and $I_B \approx \frac{I_c}{h_{FE}} = \frac{2.5mA}{100} = 25\mu A$ typical

and $V_E = I_e R_e \approx I_c R_e = (2.5mA)(.2k) = 0.5V$

and $V_B = V_E + V_F = 0.5 + 0.7 = 1.2V$ Silicon

• $R_{in} \geq 12k$: TRIAL + ERROR METHOD

$R_{in} = R_{B1} // R_{B2} // (h_{FE} + 1)R_e$; $(h_{FE} + 1)R_e \approx 20k$ here,
so $R_{B1} // R_{B2}$ large enough to yield $R_{in} \geq 12k$.

$(R_{B1} // R_{B2}) \geq 30k$ since $30k // 20k = 12k$

R_{B2} is smaller, so **TRY $R_{B2} = 40k$**

$$I_2 = \frac{V_B}{R_{B2}} = \frac{1.1V}{40k} = 27.5\mu A; I_1 = I_2 + I_B = 27.5 + 25 = 52.5\mu A$$

$$R_{B1} = \frac{V_s - V_B}{I_1} = \frac{13.8V}{52.5\mu A} = 262.9k$$

• CHECK : $R_{in} = R_{B1} // R_{B2} // (h_{FE} + 1)R_e = 292.6k // 40k // 20k = 12.75k$ OK

P. 34
Homework Set #4

$$3.) \quad X_c = \frac{1}{2\pi f C} \Rightarrow C_{in} = \frac{1}{2\pi f X_{cin}} \Big|_{10\text{Hz}} = 1.33 \times 10^{-6} \text{ F} \\ \boxed{1.33 \mu\text{F}}$$

$$C_{out} = \frac{1}{2\pi f X_{cout}} \Big|_{10\text{Hz}} = \frac{1}{(2\pi)(10)(3\text{k})} = 5.31 \times 10^{-6} \text{ F} \\ = 5.31 \mu\text{F}$$

4.) Equivalent circuit:



For this case: $R_{os} = R_{iA} = 12\text{k}$ $X_{cout} = 3\text{k}$
 $R_{oA} = R_L = 3\text{k}$ $X_{cin} = 12\text{k}$

• Input loop analysis: $V_{it} = I_{in} R_{iA} = R_{iA} \left\{ \frac{V_{os}}{(R_{os} + R_{iA}) - jX_{cin}} \right\}$

$$|V_{it}| = V_{os} \left| \frac{R_{iA}}{(R_{os} + R_{iA}) - jX_{cin}} \right|$$

$$= V_{os} \left| \left(\frac{12\text{k}}{12\text{k} [2 - j]} \right) \right| = V_{os} \sqrt{\frac{1}{5}}$$

• Output loop analysis: $V_L = I_{out} R_L = R_L \left\{ \frac{AV_{it}}{(R_{oA} + R_L) - jX_{cout}} \right\}$

$$|V_L| = |V_{it}| (15) \left\{ \left| \frac{3\text{k}}{3\text{k} (2 - j)} \right| \right\} = |V_{it}| (15) \sqrt{\frac{1}{5}}$$

• Result: $\boxed{\left| \frac{V_L}{V_{os}} \right| = EA = 15 \left(\frac{1}{\sqrt{5}} \right) \left(\frac{1}{\sqrt{5}} \right) = 3} \quad !!$

5.) Basic amplifying section:


$$A = \frac{\Delta V_c}{\Delta V_B}$$

$$V_c = V_s - I_c R_c \Rightarrow \Delta V_c = -\Delta I_c R_c$$


$$V_e = I_e R_e \Rightarrow \Delta V_e = \Delta I_e R_e$$

$$V_B = V_e + 0.7 \Rightarrow \Delta V_e = \Delta V_B$$

$$I_e = I_B + I_c \approx I_c$$

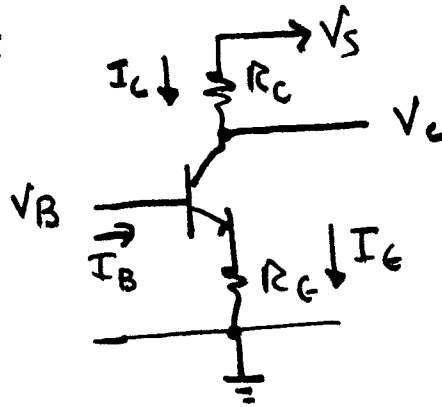
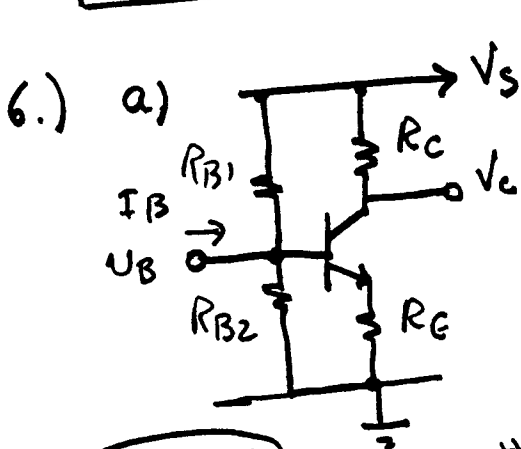
$$\therefore \frac{\Delta V_c}{\Delta V_B} = \frac{-\Delta I_c R_c}{\Delta V_e} = \frac{-\Delta I_c R_c}{\Delta I_e R_e} = \frac{-\cancel{\Delta I_c} R_c}{\cancel{\Delta I_c} R_e} = -\frac{R_c}{R_e}$$




$$R_{in} = \frac{\Delta V_B}{\Delta I_B} \quad \text{For basic amplifying section: } \Delta V_B = \Delta V_e \quad (\text{see \#5})$$

$$= \Delta I_e R_e$$

$$= (h_{fe} + 1) \Delta I_B R_e$$

$$\therefore \frac{\Delta V_B}{\Delta I_B} = (h_{fe} + 1) R_e$$

equivalent net result is:

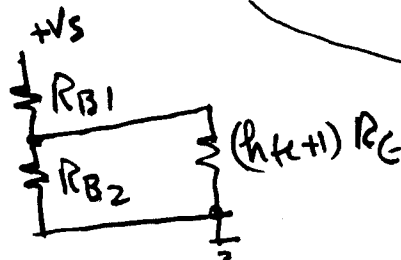


Since V_s is constant, ΔV_B is what matters, V_s = "ground" for changing signals (any constant V is "ground".)

$$\therefore R_{in} = R_{B1} // R_{B2} // (h_{fe} + 1) R_e$$

HW set 4 P.5b

6.) b. Rout :

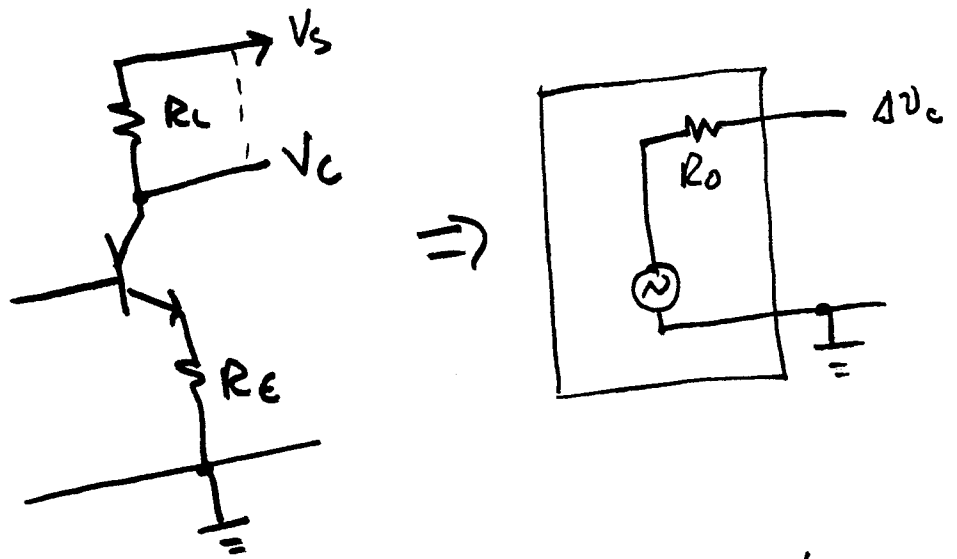

strategy : use Thevenin's theorem + approach that

$$R_o = \frac{V_o|_{\text{open}}}{I_o|_{\text{short}}}$$

Since $v_o = \Delta v_c$, $v_o|_{\text{open}} = R_c \Delta I_c$. Using the idea that

all points of constant voltage (such as v_s) are "a.c ground",

$$I_o|_{\text{short}} = \Delta I_c.$$

$$\therefore R_o = \frac{v_o|_{\text{open}}}{I_o|_{\text{short}}} = \frac{R_c \Delta I_c}{\Delta I_c} = R_c$$

P.7
H.W. set # 4

8.)

a.) Ignoring base current $\Rightarrow I_1 = I_2 = I$

$$I = \frac{V_s}{90k} = \frac{12V}{90k} = \frac{4}{30} \text{ mA}$$

$$= 133 \mu\text{A}$$

$$\begin{aligned} V_B &= I R_{B2} = 1.0V \\ V_E &= V_B - V_f = 0.3V \\ V_C &= V_s - I_C R_C = 12V - 3k = 9V \end{aligned} \quad \rightarrow \quad I_E = \frac{V_E}{R_E} = \frac{0.3V}{0.3k} = 1 \text{ mA} = I_C$$

b.) Considering base current:

- $I_1 = I_2 + I_B$
- $I_E \cong I_C = h_{FE} I_B$


- $V_B = I_2 R_{B2} = V_s - I_1 R_{B1} \Rightarrow I_1 = \frac{V_s - V_B}{R_{B1}}; I_2 = \frac{V_B}{R_{B2}}$
- $V_E = V_B - V_f$
- $V_E = I_E R_E \cong I_C R_E \Rightarrow I_B = \frac{I_E}{h_{FE}} = \frac{V_E / R_E}{h_{FE}} = \frac{(V_B - V_f)}{R_E h_{FE}}$
- $V_C = V_s - I_C R_C$

$$I_1 = I_2 + I_B \Rightarrow \left\{ \frac{V_s - V_B}{R_{B1}} = \frac{V_B}{R_{B2}} + \frac{V_B - V_f}{R_E h_{FE}} \right.$$


$$\text{By algebra} \Rightarrow V_B \left(1 + \frac{R_{B1}}{R_{B2}} + \frac{R_{B1}}{R_E h_{FE}} \right) = V_s + V_f \frac{R_{B1}}{R_E h_{FE}}$$

$$\begin{aligned} \underline{V_B} &= \frac{V_s + V_f \frac{R_{B1}}{R_E h_{FE}}}{\left(1 + \frac{R_{B1}}{R_{B2}} + \frac{R_{B1}}{R_E h_{FE}} \right)} = \underline{1.19V} \\ \underline{V_E} &= V_B - V_f = 1.19V - 0.7V = \underline{0.49V} \\ \underline{V_C} &= V_s - I_C R_C = V_s - \frac{V_E R_C}{R_E} = \underline{\underline{7.1V}} \end{aligned}$$

$$I_C = I_E = \frac{V_E}{R_E}$$

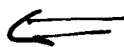

7.)

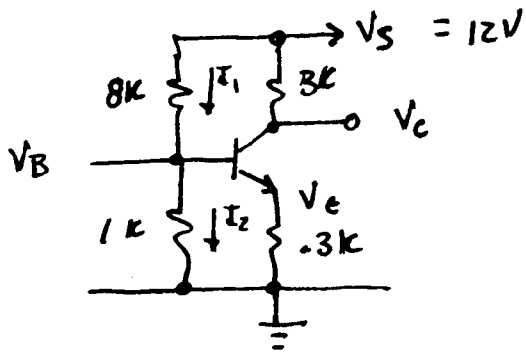

$$\text{Since } I_1 = I_2 (=I)$$

$$I = \frac{12V}{8k + 1k} = \frac{12V}{9k} = \underline{\underline{\frac{4}{3} \text{ mA}}}$$

$$\underline{\underline{V_B = I R_{B2} = \frac{4}{3} V}}$$

$$\underline{\underline{V_E = V_B - V_f = \frac{4}{3} V - 0.7V = 0.63V}}$$

$$V_C = V_S - I_C R_C \quad I_C \approx I_E ; \quad \underline{\underline{I_E = \frac{V_E}{R_E} = \frac{0.63V}{0.3k} = 2.1 \text{ mA} = I_C}}$$

$$\therefore \underline{\underline{V_C = 12V - (2.1 \text{ mA})(3k) = 5.7V}}$$

I_B is negligible for several reasons. Consider the following:

- at most $I_C = V_S / R_C = 12V / 3k = \underline{4 \text{ mA}}$

- for $I_C = 4 \text{ mA}$, $I_B \approx \frac{4 \text{ mA}}{100} = 40 \mu\text{A}$

- compared to $\frac{4}{3} \text{ mA}$ ($1333\frac{1}{3} \mu\text{A}$), $40 \mu\text{A}$ is negligible