

Homework Set 6 Physics 3500/8800

1. By use of Truth tables, show that the following are true:

a. $\overline{A \cdot B} = \overline{A} + \overline{B}$

b. $\overline{A + B} = \overline{A} \cdot \overline{B}$

c. $A \cdot 1 = A$

d. $\overline{A \cdot A} = \overline{A}$

e. $A + 1 = 1$

f. $\overline{A + A} = \overline{A}$

g. $A + 0 = A$

h. $A \cdot 0 = 0$

2. Using the most straightforward approach, design a logic circuit to provide the following:

- a. out = 1 for A = 1, or B = 1, or C = 1
- b. out = 0 for (A = 0, or B = 1) & C = 1
- c. out = 1 for A = 1 & B = 1 or A = 0 & B = 0

3. Repeat #2 using *only* 2-input NAND gates.

4. Work out the algebraic relation to accomplish the tasks of #2 using NAND gates as in #3.

5. For each Boolean algebra expression below, sketch the corresponding circuit relating the variables indicated to the output (*use only 2-input gates and inverters*):

a. $\overline{(\overline{A} \cdot \overline{B})} + C = \text{OUT}$


b. $(A + B) \cdot \overline{C} = \text{OUT}$

c. $\overline{A \cdot B} \cdot \overline{C} = \text{OUT}$


d. $\overline{[(\overline{A} \cdot \overline{B}) + (\overline{B} \cdot \overline{A})]} \cdot C = \text{OUT}$

6. Write the Boolean algebraic relation between the inputs and the outputs for the circuits shown:


a.

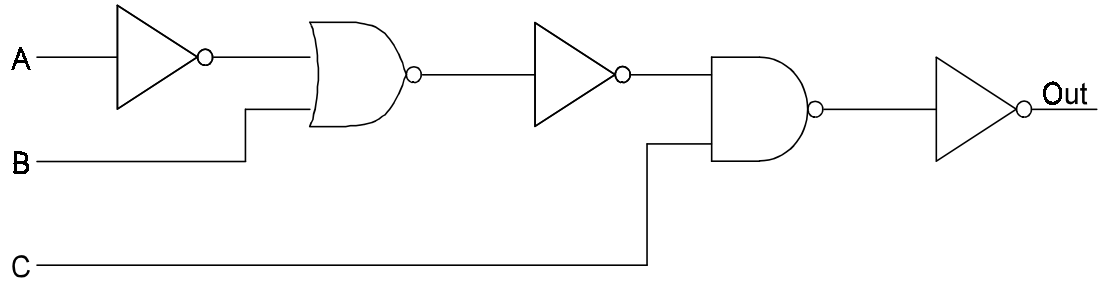


b.

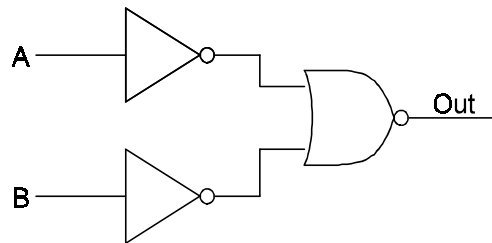

c.

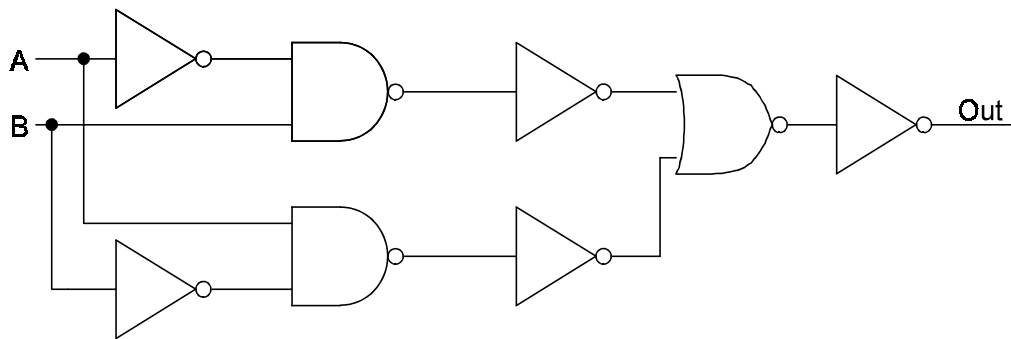

d.

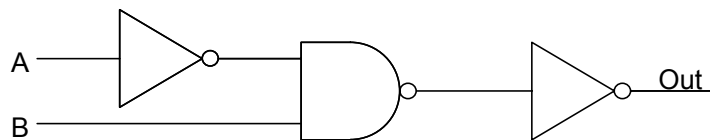

7. Draw the circuit for each of the following Boolean expressions using **only** gates of the type indicated:

a. $A \cdot B \cdot \overline{C} = \text{OUT}$, 2-input NOR gates

b. $A \cdot B \cdot \overline{C} = \text{OUT}$, 2-input NAND gates

c. $(\overline{A \cdot B}) + (\overline{B \cdot A}) = \text{OUT}$, 2-input NOR gates

d. $(\overline{A + B}) \cdot \overline{C} = \text{OUT}$, 2-input NAND gates

8. Convert the following **decimal** numbers to **binary and to hexadecimal**:

a. 42 b. 784 c. 481 d. 25 e. 106
f. 14 g. 999 h. 1024 i. 511 j. 255

9. Convert the following **hexadecimal** numbers to **binary and to decimal**:

a. 15 b. 1AC c. 2C d. EF e. A
f. 20 g. 1000 h. FFF i. 999 j. ABC

10. Perform the indicated binary arithmetic operations using **2's complement** arithmetic for any subtractions:

a. $\begin{array}{r} 1011 \\ +0101 \\ \hline \end{array}$ b. $\begin{array}{r} 11011 \\ -01100 \\ \hline \end{array}$ c. $\begin{array}{r} 1001 \\ -0110 \\ \hline \end{array}$

d. $\begin{array}{r} 11011 \\ +01100 \\ \hline \end{array}$ e. $\begin{array}{r} 101101 \\ -010110 \\ \hline \end{array}$ f. $\begin{array}{r} 101101 \\ +101001 \\ \hline \end{array}$

11. Sketch the most straightforward circuit to implement the following:

a. $\text{OUT} = 1$ only if $A = 0$, $B = 1$, and $C = 1$

b. $\text{OUT} = 0$ only if $A = 1$, $B = 1$, and $C = 0$

c. $\text{OUT} = 1$ only if $A = 1$, $B = 0$, and $C = 1$ or if $B = 1$

d. $\text{OUT} = 1$ only for $A = 0$, $B = 0$, and $C = 0$

12. Write the logic relations necessary for comparing two 2-bit binary numbers and indicating with $OUT = 1$ if they are equal. (Note that such binary numbers can be written as $A = A_1A_0$, where A_0 represents the least significant bit, and A_1 represents the most significant bit.)
13. Sketch the circuit to compare two 2-bit binary numbers and indicate by $OUT = 1$ if they are equal.
14. Write the logic relations necessary for comparing two 2-bit binary numbers and indicating with $OUT = 1$ if $A > B$. (The case $A \leq B$ should give $OUT = 0$.)
15. Add to the circuit of #13 the additional circuitry necessary to give a *second* output which is ONE if $A > B$, and which is ZERO (NOT ONE) if $A \leq B$.
16. Write the logic equation, and sketch the circuit necessary to implement the following truth table:

A	B	C	OUT
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1