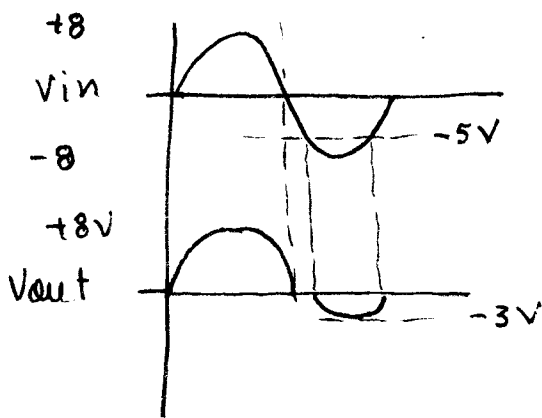


Homework Set #3 Solution


1.) Basic idea: For forward voltages, the diode has no effect on the circuit (or, it behaves like $R=0$). For reverse voltages the diode behaves like $R \rightarrow \infty$, and thus has all the voltage across it, until the reverse voltage reaches V_Z . Then the diode maintains $V_D = V_Z$, and otherwise acts like $R=0$.

In all cases, $V_{in} = V_D + V_R$ ($\odot V_{in} = V_D + V_C$ for d.)


a.)




b.)

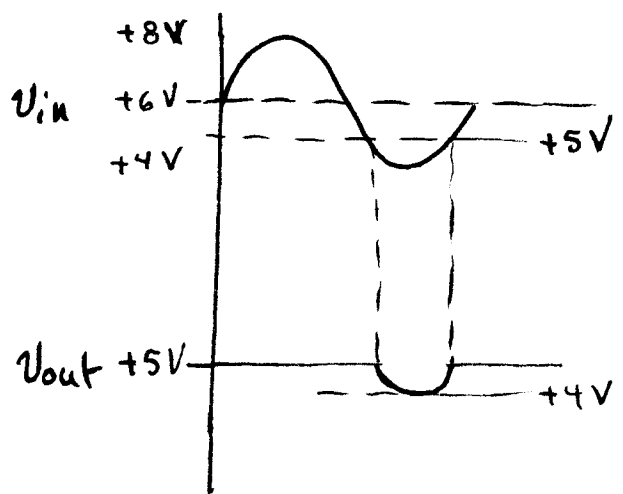

c.)

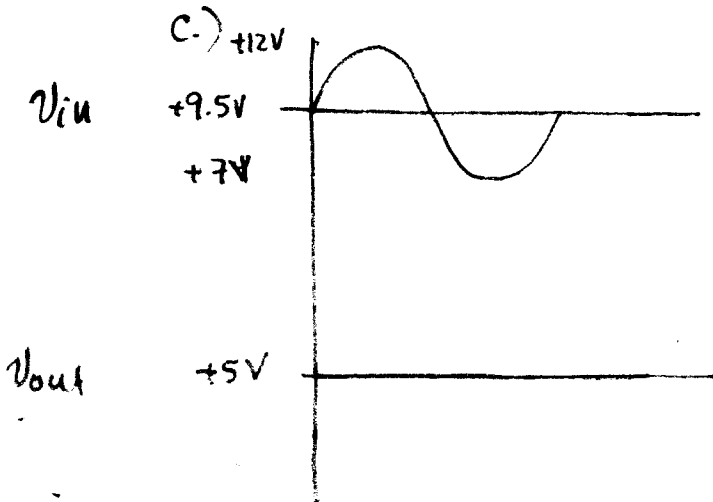


d.)

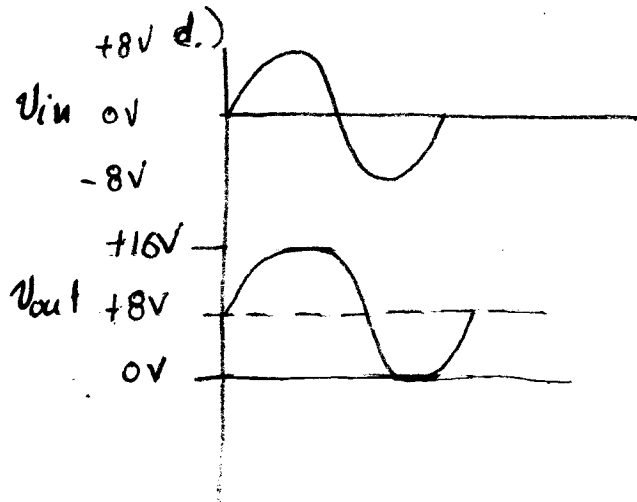



Set # 3, wout

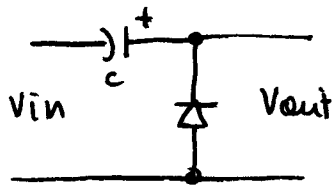1.) wout

(1d) requires more explanation: During the 1st negative half-cycle, the C charges to V_{peak} ($= 8V$, in this case). thereafter $V_{out} = V_{in} - V_c$, as shown; thus $V_{out} = V_{in}$ but shifted ~~by~~ down by V_p . (this is a "diode clamp".)



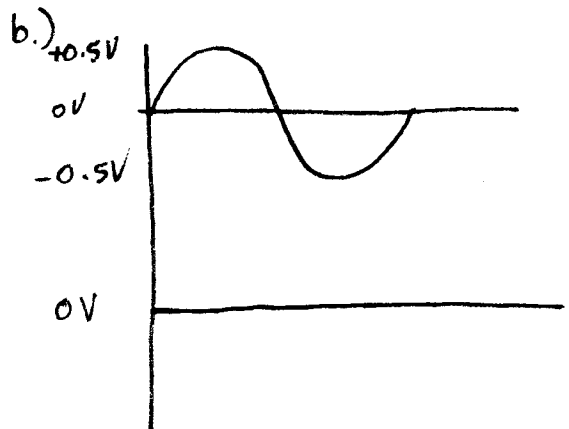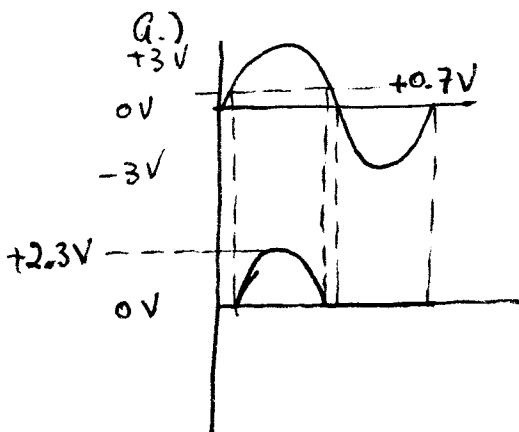2.) In this one, the diodes will not conduct in the forward direction until $V = V_{threshold}$ ($= 0.7V$, for silicon).



Set #3, cont

3.) a) Ripple = residual a.c. on an otherwise "steady" D.C.


$$\underline{\text{Ripple factor}} = \frac{\text{r.m.s. a.c. component}}{\text{D.C. component}} \left\{ \times 100\% \right\}$$

b.) Ripple results from the discharging of the filter capacitor through the load. As the charge is drained off, the voltage across the drops according to $\Delta V_c = \frac{\Delta Q}{C}$. Since the output is across the C, this is the change in V_{out} , or the ripple.

As seen above, since ~~the~~ the ripple, or $\Delta V_c = \frac{\Delta Q}{C}$, two factors can reduce it: (1) More C and (2) less ΔQ . Since the current to the load is $\frac{\Delta Q}{\Delta t} = I$, and the Δt is related to the period of the Δt unfiltered input, less ~~I~~ I leads to less ΔQ during the Δt , ~~and~~ hence more R + more C \rightarrow less ΔV_c or ripple.

c.) a full wave circuit ~~has less~~ ^{has less} Δt in comparison with a half-wave circuit.

set #3, out

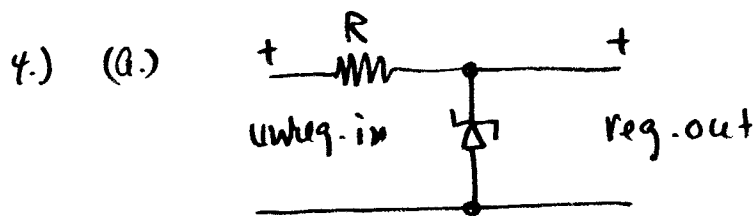

(b.) "Worst case" $V_R = 10V - 7V = 3V$

• $\min I_T = I_D + I_L @ \min V_R = (200 + 10) \text{ma} = 210 \text{ma}$

$\Rightarrow \text{Max } R = \frac{\min V_R}{\min I_T} = \frac{3V}{210 \text{ma}} = 14.28 \Omega$

choose 4.7Ω

$P_{R|_{\max}} = \frac{V_{R, \max}^2}{R} = \frac{(10V - 7V)^2}{4.7 \Omega} = 1.9W$; choose $2W$

c.) No load: R is taken care of above since all current passes through the R , load or not. But with No load, the current through the diode includes the 200ma originally sent to the load.

thus

$P_D = I_T|_{\max} V_Z = \left(\frac{10V - 7V}{4.7 \Omega}\right) 7V = 4.7W$

is less than $10W$, so o.k.

d.) • as a result of (c)'s work, Min I is 0 , and is still safe.


• Max load current is I_L such that $I_T - I_L < 10 \text{ma}$.

$I_T|_{\min} = \frac{V_{R, \min}}{R} = \frac{3V}{4.7 \Omega} = 212 \text{ma}$

so, $I_L > 202 \text{ma}$ will allow less than 10ma to diode at some times.

Physics 350/880 H.W. #3, P. 5

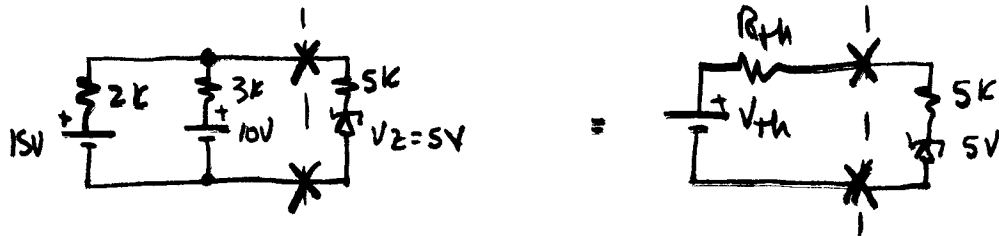
5) a. draw as shown + use Thevenin's theorem at X's:



$$R_{th} = 3k // 2k = 6k/5 = \underline{1.2k}$$

$$V_{th} = 15V - 2k \left(\frac{15-10}{2+3} \right) V = \left(15 - \frac{10}{5} \right) V = \underline{13V}$$
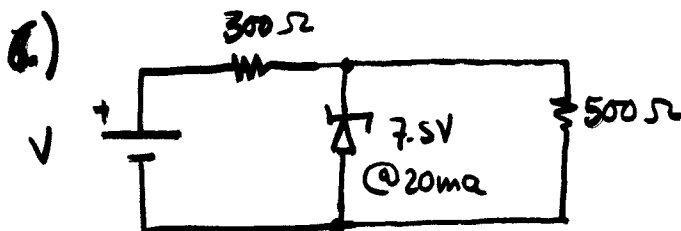
$$\therefore I_{5k} = \frac{V_{th} - V_Z}{R_{th} + 5k} = \frac{8V}{6.2k} = \underline{1.29ma}$$



a.) for minimum V_s ,

$$I_2 = 20ma$$

$$\text{AND } I_{500} = 7.5V / 500\Omega = 15ma$$

$$\therefore I_{300} = I_2 + I_{500} = 35ma$$

$$+ V_{300} = (300)(35ma) = \underline{10.5V}$$

thus, $V_{min} = V_{300} + 7.5V = 10.5 + 7.5 = \underline{18V}$

b.) $V = 20V \Rightarrow V_{300} = (20 - 7.5)V = \underline{12.5V} \Rightarrow I_{300} = \frac{12.5V}{.3k} = \underline{41.7ma}$

$$I_{300} = I_D + I_{500} ; I_{500} = 7.5V / .5k = \underline{15ma}$$

$$\therefore I_D = I_{300} - I_{500} = 41.7ma - 15ma = \underline{26.7ma}$$